

Electronics Homework

①

Series + Parallel R + C.

①. a) For $V_1 = 1.0V + V_2 = 4.0V$, V_3 must be: $10 - (1+4) = 5.0V$

So, we need to mimic this 1:4:5 ratio with our resistors with the largest resistor producing the largest V . Therefore one option is $R_1 = 50\Omega$, $R_2 = 200\Omega +$

b) $V_3 = 5.0V$

$R_3 = 250\Omega$ ($\frac{200+50}{50}$)


c) $V_s = I R_{net}$

$R_{net} = 50\Omega + 200\Omega + 250\Omega = 500\Omega$

$\therefore I = \frac{V_s}{R_{net}} = \frac{10.0V}{500\Omega} = \boxed{0.020A}$

d) $P = I^2 R_{net} = (0.020A)^2 \cdot 500\Omega = \boxed{0.20W}$

②.

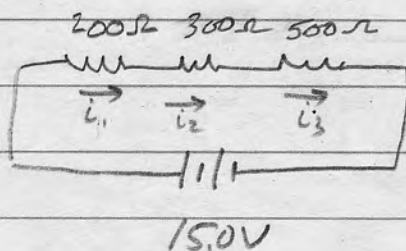

a) $V_2 = 12.0V \left(\frac{R_2}{R_{net}} \right) = 12.0V \left(\frac{300\Omega}{1000\Omega} \right)$



$\boxed{V_2 = 3.60V}$

$i_1 = i_2 = i_3 = I_{net} = \frac{V_s}{R_{net}} = \frac{12.0V}{1000\Omega} = \boxed{0.012A}$

b) $P_2 = i_2^2 R_2 = (0.012A)^2 (300\Omega) = \boxed{0.043W}$

c) $\frac{P_2}{P_T} = \frac{i_2^2 R_2}{I_{net}^2 R_{net}} = \frac{R_2}{R_{net}} = \frac{300\Omega}{1000\Omega} = 0.30$ or $\boxed{30\%}$

3

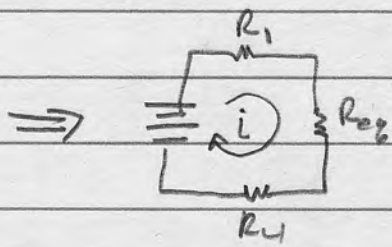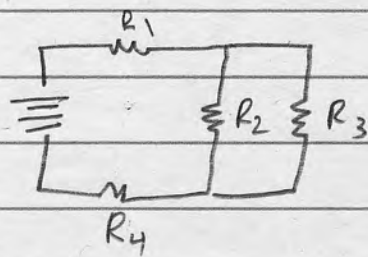

$$R_{eq} = \left(\frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$$

$$R_{eq} = \left(\frac{1}{500\Omega} + \frac{1}{200\Omega} \right)^{-1}$$

$$R_{eq} = 143\Omega$$

a) $i = \frac{V_s}{R_{eq}} = \frac{10.0\text{ V}}{(100 + 143 + 1000)\Omega} = 0.00805\text{ A}$

$V_1 = i R_1 = 0.00805\text{ A} \cdot 100\Omega = 0.805\text{ V}$

$V_2 = V_3 = i R_{eq} = 1.15\text{ V}$

$V_4 = i R_4 = 8.05\text{ V}$

b) $i_1 = i_s = i_2 + i_3 = 0.00805\text{ A}$

$i_3 = i_4$



$i_2 = \frac{V_2}{R_2} = \frac{1.15\text{ V}}{500\Omega} = 0.0023\text{ A}$

$i_3 = i_4 = \frac{V_3}{R_3} = \frac{1.15\text{ V}}{200\Omega} = 0.00575\text{ A}$

c) $P = I^2 R = (0.0023\text{ A})^2 \cdot 500\Omega = 0.0026\text{ W}$

d) $V_{3-4} = 10.0\text{ V} - V_1 = 10.0\text{ V} - 0.805\text{ V} = 9.20\text{ V}$

4

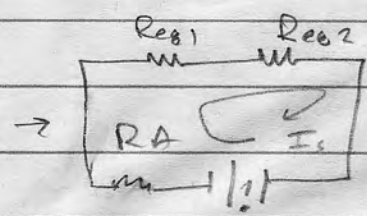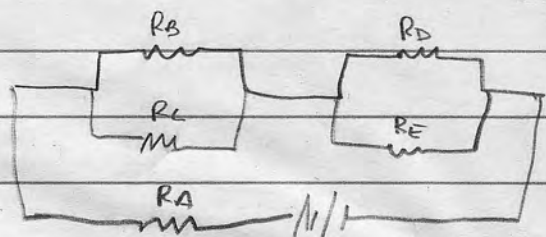

$R_{eq1} = \left(\frac{1}{2000} + \frac{1}{4000} \right)^{-1} = 1333\Omega$

$R_{eq2} = \left(\frac{1}{2000} + \frac{1}{1000} \right)^{-1} = 667\Omega$

$R_{eq3} = 1333\Omega + 667\Omega + 1000\Omega = 3000\Omega$

$V_s = I_s R_{eq} \Rightarrow I_s = \frac{V_s}{R_{eq}} = \frac{24\text{ V}}{3000\Omega} = 0.0080\text{ A}$

4, cont.

$$a) P = I^2 R_{eq} = (0.0080 A)^2 \cdot 1333 \Omega = \boxed{0.085 W}$$

$$b) I = \boxed{0.0080 A}$$

$$c) V_A = I R_A = 0.0080 A \cdot 1000 \Omega = \boxed{8.0 V}$$

$$d) V_D = I R_{eq2} = 0.0080 A \cdot 667 \Omega = \boxed{5.34 V}$$

$$e) V_{S4} = 24 - V_A = 24 - 8 = \boxed{16.0 V}$$

⑤

$$a) V = iR \Rightarrow R = \frac{V}{i} = \frac{1.00 V}{50 \times 10^{-6} A} = 20,000 \Omega = \boxed{20 k\Omega}$$

b) 1% error = $0.01 \cdot 50 \mu A = 0.50 \mu A$

$$R = \frac{V}{i} = \frac{1.0 V}{0.50 \times 10^{-6}} = 2,000,000 \Omega = \boxed{2 M\Omega}$$

⑥

$$i = I_{init} e^{-t/RC} \Rightarrow \frac{i}{I_{init}} = e^{-t/RC} \Rightarrow t = -RC \ln \frac{i}{I_{init}}$$

when 1% charged $i/I_{init} = 1/100 = 0.01$

$$\therefore -R \cdot (0.035 \times 10^{-6} F) \ln(0.01) = t$$

a) $R = 10 \times 10^6 \Omega$; $t = \boxed{1.61 s}$

b) $R = 1 \times 10^6 \Omega$; $t = \boxed{0.161 s}$ (161 ms)

c) $R = 10^3 \Omega$; $t = \boxed{1.61 \times 10^{-4} s}$ (161 μs)

⑦

$$a) R \cdot C = (50 \times 10^3 \Omega) \cdot (0.015 \times 10^{-6} F) = \boxed{7.50 \times 10^{-4} s = 0.75 ms}$$

$$b) I_{init} = \frac{V}{R} = \frac{25 V}{50,000 \Omega} = 0.00050 A$$

for charging

$$\begin{cases} i = I_{init} e^{-t/RC} \\ V_R = V_{init} e^{-t/RC} \\ V_C = V_{init} - V_C \end{cases}$$


discharge

$$\begin{cases} V_C = V_0 e^{-t/RC} \\ V_R = -V_C \\ i = V_R/R \end{cases}$$

	A	B	C	D
1	Charging			
2	t	i	Vc	Vr
3	ms	uA	V	V
4	0	500.00	25.00	0.00
5	1	131.80	6.59	18.41
6	2	34.74	1.74	23.26
7	3	9.16	0.46	24.54
8	4	2.41	0.12	24.88
9	5	0.64	0.03	24.97
10	10	0.00	0.00	25.00
11				
12				
13	Discharge			
14	t	Vc	Vr	i
15	ms	V	V	uA
16	0	25.00	-25.00	-500.00
17	1	6.59	-6.59	-131.80
18	2	1.74	-1.74	-34.74
19	3	0.46	-0.46	-9.16
20	4	0.12	-0.12	-2.41
21	5	0.03	-0.03	-0.64
22	10	0.00	0.00	0.00
23				
24	B4=500*EXP((-A4/1000)/0.00075)			
25	C4=25*EXP(-(A4/1000)/0.00075)			
26	D4=25-C4			
27				
28	B16=\$D\$10*EXP((-A16/1000)/0.00075)			
29	C16=-B16			
30	D16=1000000*(C16/50000)			


Op-Amps

① There are several options. Here's one:

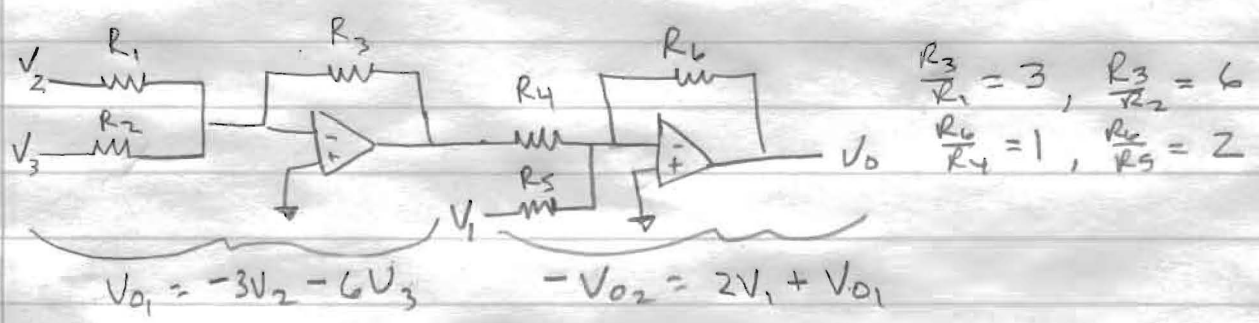

$V_{O1} = -3V_2 - 6V_3$ $-V_{O2} = 2V_1 + V_{O1}$

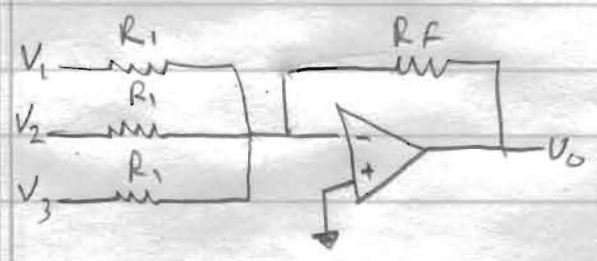② Here is one option, we need to accomplish this math: $V_0 = \frac{1}{1000} \left(\frac{V_1 + V_2 + V_3}{3} \right) = \frac{V_1 + V_2 + V_3}{3000}$



we need $\frac{R_F}{R_1} = \frac{1}{3000}$
 perhaps $R_F = 1K\Omega + R_1 = 3M\Omega$

* in this case $-V_0 = \frac{V_1 + V_2 + V_3}{3000}$, we could add a second op amp to change the sign of V_0

③ We have 2 addition operations in series.

for the first op amp:

$$V_{O1} = - \left(\frac{R_{F1}}{R_1} V_1 + \frac{R_{F1}}{R_2} V_2 \right)$$

for the second op amp:

$$-V_{O2} = \frac{R_{F2}}{R_4} \cdot V_{O1} + \frac{R_{F2}}{R_3} V_3$$

$$-V_{O2} = \frac{R_{F2}}{R_4} \left(-\frac{R_{F1}}{R_1} V_1 - \frac{R_{F1}}{R_2} V_2 \right) + \frac{R_{F2}}{R_3} V_3$$

$$-V_{O2} = -V_1 \left(\frac{R_{F1} R_{F2}}{R_1 R_4} \right) - V_2 \left(\frac{R_{F1} R_{F2}}{R_2 R_4} \right) + V_3 \left(\frac{R_{F2}}{R_3} \right)$$

So


$$V_0 = V_1 \left(\frac{R_{F1} R_{F2}}{R_1 R_4} \right) + V_2 \left(\frac{R_{F1} R_{F2}}{R_2 R_4} \right) - V_3 \left(\frac{R_{F2}}{R_3} \right)$$

③ b) Inserting Values :

$$V_o = V_1 \left(\frac{200K \cdot 400K}{200K \cdot 400K} \right) + V_2 \left(\frac{200K \cdot 400K}{50K \cdot 400K} \right) - V_3 \left(\frac{400K}{10K} \right)$$

$$\therefore \boxed{V_o = V_1 + 4V_2 - 40V_3}$$

④

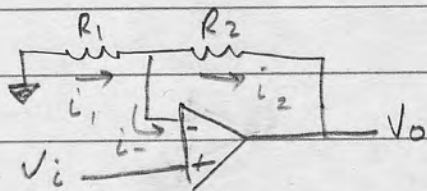

$$V_i = V_+$$

$$V_+ = V_- = V_i$$

$$i_1 = i_2 + i_- \quad \text{but } i_- = 0$$


$$i_1 = i_2$$

$$\therefore \frac{0 - V_i}{R_1} = \frac{V_i - V_o}{R_2} \Rightarrow -\frac{V_i}{R_1} = \frac{V_i - V_o}{R_2}$$

$$-\left(\frac{R_2}{R_1}\right) V_i = V_i - V_o$$

$$\boxed{V_o = V_i + \frac{R_2}{R_1} V_i = \left(\frac{R_1 + R_2}{R_1}\right) V_i}$$

⑤

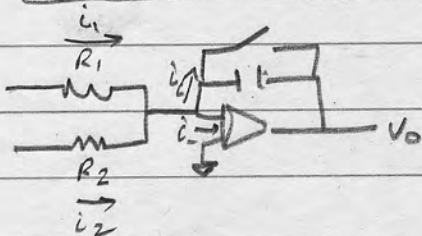

$$i_1 + i_2 = i_c + i_-$$

$$i_1 + i_2 = i_c \quad i_c = -C \frac{dV_o}{dt}$$

$$\frac{V_1 - V_-}{R_1} + \frac{V_2 - V_-}{R_2} = -C \frac{dV_o}{dt}$$


$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = -C \frac{dV_o}{dt}$$

$$dV_o = -\frac{1}{C} \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right) dt = -\frac{1}{0.01\mu F} \left(\frac{V_1}{20M\Omega} + \frac{V_2}{5M\Omega} \right) dt$$

$$dV_o = -\left(\frac{V_1}{0.2S} + \frac{V_2}{0.05S} \right) dt$$

$$V_o = -\int_0^t \left(\frac{V_1}{0.2S} + \frac{V_2}{0.05S} \right) dt \quad \text{or } V_o = -\int_0^t (5S^{-1} V_1 + 20S^{-1} V_2) dt$$

(6)

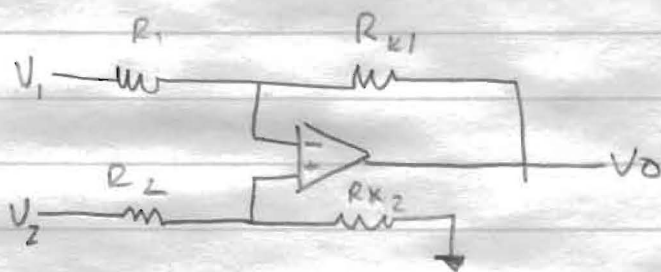

$$R_1 = R_2 = R_{k1} = R_{k2}$$

$$\frac{V_1 - V_-}{R_1} = \frac{V_- - V_o}{R_{k1}} \quad \text{but } R_1 = R_{k1}$$

$$\times \text{ so } V_1 - V_- = V_- - V_o$$

$$\frac{V_2 - V_+}{R_2} = \frac{V_+ - 0}{R_{k2}} \quad \text{but } R_2 = R_{k2}$$

$$\times \text{ so } V_2 - V_+ = V_+$$

$$V_+ = \frac{V_2}{2} \quad \text{and} \quad V_- = \frac{V_1 - V_o}{2} \quad \text{and } V_+ = V_-$$

$$\text{so } \frac{V_2}{2} = \frac{V_1 - V_o}{2}$$

$$\text{and } V_2 = V_1 - V_o$$

$$\text{or } \boxed{V_o = V_1 - V_2}$$

A/D

①

absolute

Relative

a) $\frac{10V}{2^8} = 0.039V$

$\frac{0.039V}{5V} \cdot 100\% = 0.78\%$

b) $\frac{10V}{2^{12}} = 0.00244V$

0.0488%

c) $\frac{10V}{2^{16}} = 0.000153$

0.00305%

②

abs

rel

a) $\frac{10V}{2^8} = 0.039V$

$\frac{0.039V}{0.2V} \cdot 100\% = 19.5\%$


b) $\frac{10V}{2^{12}} = 0.00244V$

1.22%

c) $\frac{10V}{2^{16}} = 0.000153V$

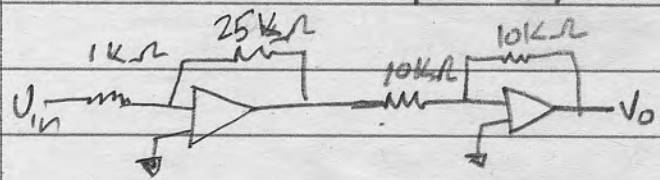0.0763%

if we amplify the signal by 25x, our % uncertainty will be as in pt a, This circuit will do it.



③ $\therefore$ AD can't respond faster than $15 \mu s$, or in terms of frequency: $\frac{1}{8 \mu s} = 66,600 \text{ Hz}$

To accomplish Nyquist, maximum rate is

$$\frac{1}{2} (66,600 \text{ Hz}) = \underline{33,300 \text{ Hz}} \text{ or sample once every } 30 \mu s$$